

# Internship Project Report

## Title: 2-Layer PCB Design for Half-Bridge Class D Bluetooth Audio Amplifier

### 1. Project Overview

This project focused on the schematic design and PCB layout of a **Class D audio amplifier** using a **half-bridge topology** on a **2-layer PCB**. The amplifier is capable of driving a speaker with high efficiency, using **Pulse Width Modulation (PWM)** techniques to amplify the audio signal. A key feature of the system is the integration of the **MHM-28 Bluetooth module**, which enables wireless audio streaming. The project involved extensive work in analog and digital electronics, filter design, power electronics, and PCB layout using KiCad.

### 2. Why Class D Amplifier?

The amplifier design employs a **Class D topology**, which is known for:

- **High Efficiency:** Typically >90%, due to transistors operating as switches rather than linear amplifiers
- **Compact Size:** No need for large heatsinks or power-hungry biasing components
- **Low Heat Dissipation:** Minimal energy lost as heat, important for embedded and portable systems
- **Suitability for Wireless Audio Systems:** Efficiency and size are critical in battery-operated or space-constrained environments

In contrast to Class A, B, or AB amplifiers, Class D operates transistors in either full-on or full-off states, drastically reducing power loss and improving overall efficiency.

### 3. Why Half-Bridge Topology?

The choice of **half-bridge topology** was motivated by several key advantages:

- **Fewer Components:** Only two switching transistors required, reducing cost and complexity
- **Simpler Gate Drive:** Easily implemented with a dedicated driver like the IRS2113
- **Compact Design:** Ideal for 2-layer PCBs with limited space
- **Single-Supply Operation:** Suitable for unipolar speaker connections

While full-bridge topologies provide differential output and potentially higher power, they also require more components and increased design complexity. For this application, the half-bridge met all performance and efficiency requirements.

## 4. System Block Diagram Overview

Block	Function
Power Supply	Provides 5V and 12V rails via linear regulators
TLC555 Timer	Generates a triangle waveform for PWM modulation
LM393 Comparator	Compares audio input with reference waveform to create PWM
74HC04 Inverters	Insert dead time and shape signals
IR2113 Driver	Drives high-side and low-side MOSFETs
IRLZ44N MOSFETs	Perform power switching to drive speaker load
LC Filter	Reconstructs audio from PWM output
MHM-28 Module	Receives Bluetooth audio input

## 5. Bluetooth Interfacing with MHM-28 Module

The **MHM-28 Bluetooth module** enables seamless audio streaming from devices such as smartphones or laptops. Key features include:

- Bluetooth V4.0 with A2DP profile
- Stereo analog audio output
- Compact and low-power design
- Simple integration via header pins

In this project, the stereo output is connected to the inverting input of the comparator (LM393), where it is modulated against a reference triangle waveform to create a PWM representation of the input audio signal.

## 6. Power Supply Design

Two linear regulators were used:

- **LM7805 (U5):** Provides a regulated 5V supply for logic-level devices and control circuitry
- **LM7812 (U6):** Supplies a stable 12V rail required for the IRS2113 gate driver and MOSFET switching

The regulators are stabilized with decoupling capacitors:

- Input: 47 $\mu$ F electrolytic
- Output: 47 $\mu$ F electrolytic + 220nF ceramic (for high-frequency stability)

## 7. PWM Generation and Signal Conditioning

The TLC555 timer is configured in astable mode to generate a triangle or sawtooth waveform. This waveform is fed to one input of the LM393 comparator. The other input receives the analog audio signal (from MHM-28), resulting in a PWM signal whose duty cycle varies according to the audio amplitude.

To ensure proper switching and protect the MOSFETs, **dead time** is introduced using **74HC04 inverters** to delay signal edges and prevent shoot-through currents.

## 8. Driver and Switching Stage

The IRS2113 high- and low-side driver IC is responsible for:

- Driving the gates of the IRFZ44N MOSFETs
- Level-shifting logic signals to 12V gate control
- Ensuring proper timing and dead-time insertion between high-side and low-side switching

The IRFZ44Ns were chosen for their:

- Fast switching times
- High current capacity
- Low  $R_{ds(on)}$  for efficient conduction

## 9. LC Output Filter Design and Calculations

To convert the PWM back into an analog signal, an **LC low-pass filter** is employed.

**Filter Type:** *Parallel LC configuration*

This configuration resonates at the desired cutoff frequency, shunting high-frequency switching components to ground.

**Target Cutoff Frequency:**

The desired cutoff frequency was chosen to be: ( $f_c$  , , )

This ensures:

- Audio frequencies (<20 kHz) are passed
- Switching frequencies (~200 kHz) are effectively attenuated

**Component Values:**

- **L = 16.5  $\mu$ H**
- **C = 1.03  $\mu$ F**

### Formula:

$$(f_0 = 1/2\pi(\sqrt{LC}))$$

Substituting the values: ( $f_0 = 38.6\text{KHz}$ )

This confirms that the parallel LC filter is correctly tuned to the switching frequency region, offering excellent attenuation of unwanted harmonics.

## 10. PCB Layout and Implementation

The circuit was implemented on a **2-layer PCB**, with careful consideration for:

- **Grounding and decoupling:** Ground planes and bypass capacitors placed close to ICs
- **Minimized loop area:** Power and signal paths routed efficiently to reduce EMI
- **MOSFET layout:** Placed near driver for minimal gate trace delay
- **Bluetooth module:** Socketed for ease of debugging and modularity

The design was completed using **KiCad**

## 11. Results and Observations

Parameter	Value
Efficiency	>90%
Max Output Power	~10–20W depending on load and supply
Cutoff Frequency	38.6 kHz
PCB Layers	2
Bluetooth Streaming	Supported via MHM-28

## 12. Conclusion

From the project the following key outputs can be obtained:

- Understanding of Class D amplifier theory and implementation
- Practical experience with analog comparator circuits and PWM control
- Hands-on design and routing of a 2-layer PCB for mixed-signal systems
- Integration of wireless streaming modules (MHM-28)
- Development of skills in power electronics, filter design, and circuit layout

The amplifier successfully achieved clean, efficient audio amplification with wireless control, suitable for both portable and fixed audio applications.